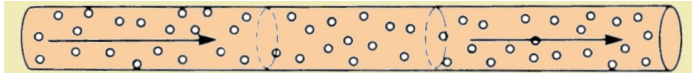



Write paragraphs describing each picture using the given words.

1.

- electrons
- current
- direction
- negative
- positive




2.

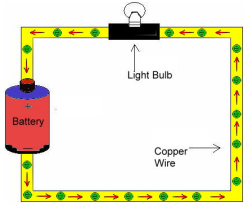


- Circuit
- electricity
- battery
- source
- resistor

3.

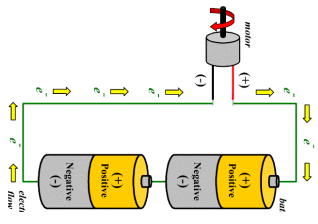


- volts
- pressure
- current
- More batteries
- Motor speed

4.

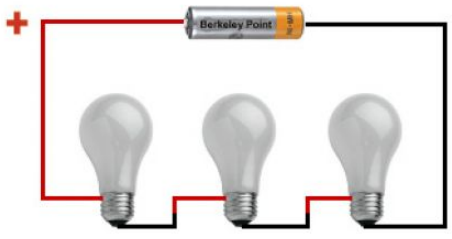

- Series
- bulbs
- Current
- if one burns out
- brightness

5.

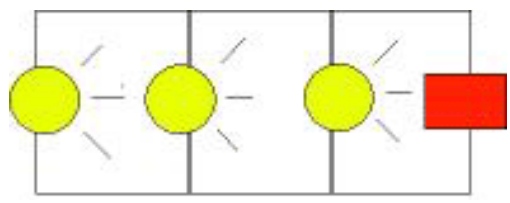

- parallel
- bulbs
- current
- If one burns out
- brightness